

**SREE VIDYANIKETHAN ENGINEERING COLLEGE**

(An Autonomous Institution, Affiliated to JNTUA, Ananthapuramu)

**II B.Tech I Semester (SVEC-19) Regular Examinations February – 2021****SWITCHING THEORY AND LOGIC DESIGN****[ Electronics and Communication Engineering, Electronics and Instrumentation Engineering ]****Time: 3 hours****Max. Marks: 60****Answer One Question from each Unit****All questions carry equal marks****UNIT-I**

- |    |    |   |         |    |     |     |
|----|----|---|---------|----|-----|-----|
| 1. | a) | Express the function $F = A + \bar{B}C$ in canonical SOP and POS.   | 6 Marks | L2 | CO1 | PO1 |
|    | b) | List the first 16 numbers in base 12; use the letters A and B to represent the last two digits. Convert the number $(456)_{12}$ to base 8 | 6 Marks | L3 | CO1 | PO3 |

**(OR)**

- |    |    |  |         |    |     |     |
|----|----|--|---------|----|-----|-----|
| 2. | a) | Generate even parity hamming code for the data word 10011010.  | 4 Marks | L4 | CO1 | PO4 |
|    | b) | i) Simplify the given Boolean expression<br>$f = ABC + \bar{A}\bar{B}C + A\bar{B} + ABC + \bar{A}\bar{B}\bar{C}$ ii) Perform the subtraction using 10 <sup>th</sup> complements.<br>i) $(1000)_{10} - (756)_{10}$ ii) $(10)_{10} - (100)_{10}$ | 8 Marks | L2 | CO1 | PO2 |

**UNIT-II**

- |    |    |  |         |    |     |     |
|----|----|--|---------|----|-----|-----|
| 3. | a) | Implement the following function in multi-level NAND<br>$F = ABC + \bar{A}BC + ABD + \bar{A}\bar{B}D$                                | 6 Marks | L3 | CO1 | PO2 |
|    | b) | Obtain the simplified expression in POS, implement with NOR gates $F(w,x,y,z) = \sum m(1, 2, 4, 11, 12, 13) + \sum d(0, 3, 6, 10)$ . | 6 Marks | L4 | CO1 | PO4 |

**(OR)**

- |    |    |   |         |    |     |     |
|----|----|---|---------|----|-----|-----|
| 4. | a) | Determine essential prime implicants given Boolean expression using tabulation method $F = ACD + BCD + \bar{B}CD + A\bar{C}D$ . | 6 Marks | L3 | CO1 | PO2 |
|    | b) | Simplify the expression in SOP<br>$F(w,x,y,z) = \sum m(0, 3, 4, 5, 7) + \sum d(8, 9, 10, 11, 12, 13, 14, 15)$ .                 | 6 Marks | L4 | CO1 | PO4 |

**UNIT-III**

- |    |    |   |         |    |     |     |
|----|----|---|---------|----|-----|-----|
| 5. | a) | Implementing the logic function using a multiplexer $2^{N-1}$ input line, where N is the number of variables in the function<br>$F(A, B, C, D) = \sum m(4, 5, 6, 7, 8, 13, 14, 15)$ . | 6 Marks | L3 | CO1 | PO4 |
|    | b) | Define encoder. Design Octal to Binary encoder.   | 6 Marks | L4 | CO2 | PO2 |

**(OR)**

- |    |    |  |         |    |     |     |
|----|----|--|---------|----|-----|-----|
| 6. | a) | Design a BCD to Decimal Adder Combinational circuit.                         | 6 Marks | L2 | CO2 | PO1 |
|    | b) | Construct 5 to 32 decoder using one 2 to 4 decoder and four 3 to 8 decoders. | 6 Marks | L4 | CO2 | PO2 |

**UNIT-IV**

- |    |    |  |         |    |     |     |
|----|----|--|---------|----|-----|-----|
| 7. | a) | Convert JK Flip Flop to T Flip Flop.   | 6 Marks | L3 | CO2 | PO3 |
|    | b) | Design a Universal Shift Register and explain the operation with neat diagram. | 6 Marks | L3 | CO1 | PO6 |

**(OR)**

- |    |    |   |         |    |     |     |
|----|----|---|---------|----|-----|-----|
| 8. | a) | Design 3 Bit UP/Down Synchronous counter using T Flip Flop. | 6 Marks | L3 | CO2 | PO6 |
|    | b) | Design a 5 Bit Ring counter and explain the operation.      | 6 Marks | L3 | CO2 | PO6 |

### UNIT-V

- |             |    |  |         |    |     |     |
|-------------|----|--|---------|----|-----|-----|
| 9.          | a) | A combinational circuit is defined by the function $F_1(A, B, C) = \sum_m (3, 5, 6, 7)$ $F_2 = \sum_m (0, 2, 4, 7)$ . Implement the circuit with PLA having 3 inputs, 4 product terms and two outputs. | 6 Marks | L3 | CO3 | PO2 |
|             | b) | Realize a Logic function using $F(A, B, C) = \sum_m (2, 4, 5, 6)$ using Hazard Free logic gate network.  | 6 Marks | L2 | CO3 | PO7 |
| <b>(OR)</b> |    |  |         |    |     |     |
| 10          | a) | Distinguish the following.<br>i) PROM.                      ii) PAL.                      iii) PLA.  | 6 Marks | L1 | CO4 | PO2 |
|             | b) | Implement the following function using PROM<br>$F_1(A, B, C) = \sum_m (0, 1, 2)$ $F_2 = \sum_m (4, 5, 6, 7)$ .   | 6 Marks | L3 | CO3 | PO2 |

