

**SREE VIDYANIKETHAN ENGINEERING COLLEGE**

(An Autonomous Institution, Affiliated to JNTUA, Ananthapuramu)

**II B.Tech II Semester (SVEC-19) Regular Examinations August – 2021****ELECTRONIC CIRCUIT ANALYSIS AND DESIGN****[ Electronics and Communication Engineering, Electronics and Instrumentation Engineering ]**

Time: 3 hours

Max. Marks: 60

**Answer One Question from each Unit**  
**All questions carry equal marks**

**UNIT-I**


1. a) Derive an expression for lower cut-off frequency of the BJT amplifier due to the effect of input coupling capacitor. 6 Marks L4 CO1 PO1
  - b) “To achieve larger input impedances and current amplification factor Darlington pair is used”. 6 Marks L3 CO1 PO2
- Discuss on the above statement by giving suitable expressions with your analytical skills on multistage amplifiers.

**(OR)**

2. a) Develop an expression for voltage gain, input and output impedances of common source MOSFET amplifier. 6 Marks L4 CO1 PO3
- b) Describe the small signal model of MOSFET at low-frequency. 6 Marks L2 CO1 PO1

**UNIT-II**

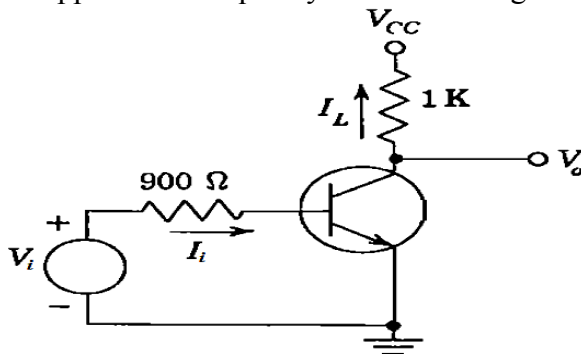3. a) The hybrid- $\pi$  parameters of the transistor used in the circuit shown are given at room temperature:  $g_m = 50\text{mA/V}$ ,  $r_{bb'} = 100\Omega$ ,  $r_{b'e} = 1\text{K}\Omega$ ,  $r_{b'c} = 4\text{M}\Omega$ ,  $r_{ce} = 80\text{K}\Omega$ ,  $C_c = 3\text{pF}$ ,  $C_e = 100\text{pF}$ . Using Miller's theorem and approximate analysis, compute the upper 3-dB frequency of the current gain  $A_i = I_L/I_i$ .



- b) Derive the expression for voltage gain of an emitter follower circuit at high frequencies. 6 Marks L4 CO2 PO2
- (OR)**
4. a) Derive the expression for Hybrid- $\pi$  conductance of common emitter transistor. 6 Marks L4 CO2 PO2
  - b) Derive the expression for CE Short Circuit Current Gain  $A_i$  as a function of frequency. Draw the frequency Response Curve. 6 Marks L4 CO2 PO2

**UNIT-III**

5. a) Elucidate the concept of negative feedback with neat block diagram and give the outlines of each block. 6 Marks L2 CO3 PO1
- b) The open loop gain of an amplifier is  $A = 5 \times 10^4$ . If the open loop gain decreases by 10%, the closed loop gain must not be change by more than 0.1%. Determine the required value of the feedback transfer function ( $\beta$ ) and the closed loop gain ( $A_f$ ). 6 Marks L3 CO3 PO2

(OR)

- |    |    |   |         |    |     |     |
|----|----|---|---------|----|-----|-----|
| 6. | a) | Derive the expressions for input and output impedance of current-series feedback amplifier.   | 6 Marks | L4 | CO3 | PO2 |
|    | b) | A voltage-series feedback amplifier employs a basic amplifier with input and output resistances each of $2k\Omega$ and gain $A = 1000$ V/V. The feedback factor $\beta = 0.1$ V/V. Find the gain $A_f$ , the input resistance $R_{if}$ , and the output resistance $R_{of}$ of the closed loop amplifier. | 6 Marks | L3 | CO3 | PO2 |

**UNIT-IV**

- |    |    |   |         |    |     |     |
|----|----|---|---------|----|-----|-----|
| 7. | a) | Derive the expression for frequency of oscillation of Wien bridge oscillator using BJT. | 6 Marks | L3 | CO3 | PO2 |
|    | b) | Derive the expression for frequency of oscillations of Hartley oscillator.              | 6 Marks | L3 | CO3 | PO2 |

(OR)

- |    |    |   |         |    |     |     |
|----|----|---|---------|----|-----|-----|
| 8. | a) | State and explain Barkhausen criterion to be satisfied to get the sustained oscillations.                       | 6 Marks | L2 | CO3 | PO1 |
|    | b) | Derive the expression for frequency of oscillations and gain condition for RC phase shift oscillator using BJT. | 6 Marks | L4 | CO3 | PO2 |

**UNIT-V**

- |    |    |  |         |    |     |     |
|----|----|--|---------|----|-----|-----|
| 9. | a) | A power transistor operating in class A transformer coupled amplifier is to deliver a maximum of 5W to a $4\Omega$ load (i.e. $R_L = 4\Omega$ ). The quiescent point is adjusted for symmetrical clipping, and the collector supply voltage is $V_{CC} = 20V$ . Assume ideal characteristics with $V_{min} = 0$ . Determine:<br>i) Transformer turns ratio.<br>ii) Peak collector current.<br>iii) Quiescent operating point.<br>iv) Collector-circuit efficiency. | 6 Marks | L3 | CO4 | PO2 |
|    | b) | Explain the origin of crossover distortion. Describe the method to minimize this distortion.   | 6 Marks | L2 | CO4 | PO1 |

(OR)

- |    |    |   |         |    |     |     |
|----|----|---|---------|----|-----|-----|
| 10 | a) | Derive an expression for bandwidth of a single stage tuned amplifier.   | 6 Marks | L3 | CO4 | PO2 |
|    | b) | Write short notes on:<br>i) Class S Power amplifier.<br>ii) Heat sinks. | 6 Marks | L1 | CO4 | PO1 |

