

**SREE VIDYANIKETHAN ENGINEERING COLLEGE**

(An Autonomous Institution, Affiliated to JNTUA, Ananthapuramu)


**I B.Tech II Semester (SVEC-19) Regular Examinations, December - 2020****ELECTRIC CIRCUITS****[ Electrical and Electronics Engineering ]**

Time: 3 hours

Max. Marks: 60

**Answer One Question from each Unit****All questions carry equal marks****UNIT-I**


1. a) What is the total equivalent resistance of the circuit across 12V Source? 6 Marks L3 CO1 PO2

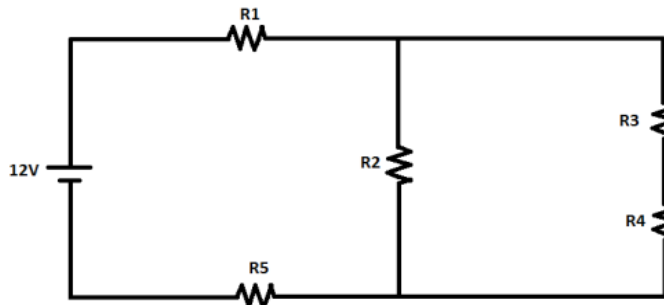Given that  $R_1=5\Omega$ ,  $R_2=3\Omega$ ,  $R_3=1\Omega$ ,  $R_4=2\Omega$ ,  $R_5=2\Omega$ .

- b) Give the details of Source Transformation technique with an example. 6 Marks L3 CO1 PO3

**(OR)**

2. a) Explain clearly about Star-delta and delta-Star transformation. 6 Marks L3 CO1 PO3  
b) Find the Voltage drop across the  $2\Omega$  resistor. 6 Marks L3 CO1 PO2

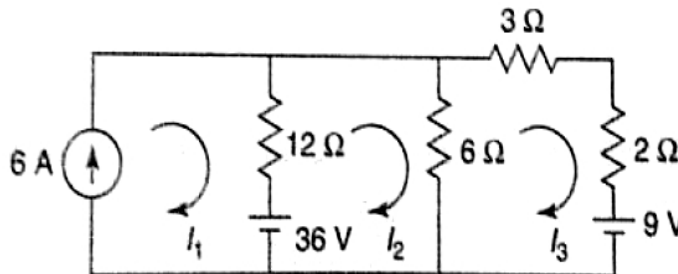**UNIT-II**


3. a) Determine the DC response of RL and RC circuit and sketch the voltage transients. 6 Marks L2 CO2 PO1  
b) Derive the expression for bandwidth of series resonating circuit and its relation with Q. 6 Marks L1 CO2 PO1

**(OR)**

4. a) In a series RLC circuit with variable capacitance, the current is at maximum value with capacitance of  $20\mu\text{F}$  and the current reduces to 0.707 times the maximum value with a capacitance of  $30\mu\text{F}$ . Find the values of R and L. What is the bandwidth of the circuit if supply voltage is  $V(t)=20\sin(6280t)$  volts? 6 Marks L2 CO2 PO1  
b) Elucidate measurement of power and power factor of a balanced 3 phase load with neat sketch using two Wattmeter method. 6 Marks L2 CO2 PO1


### UNIT-III

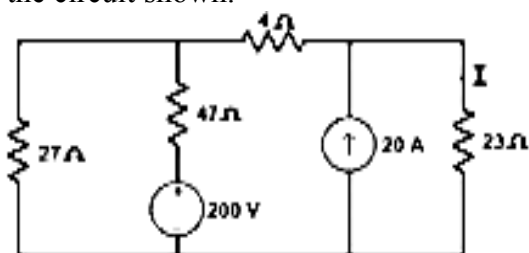5. a) Compute the current in 23 Ohm resistor using super position theorem for the circuit shown. 6 Marks L2 CO3 PO1



- b) State and explain Thevenin's theorem with an example. 6 Marks L2 CO3 PO3  
(OR)

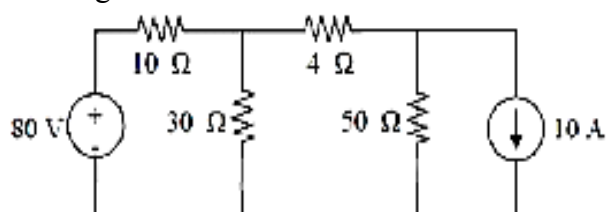6. a) Verify the Tellegen's theorem for the circuit shown. 6 Marks L1 CO3 PO2



- b) Explain duality in electrical engineering. State the steps followed in finding the dual of a network. 6 Marks L3 CO3 PO3

### UNIT-IV

7. a) i) What is mutual inductance? How it is related with the self-inductance of coils. 6 Marks L1 CO4 PO2  
ii) What is the equivalent inductance if inductor  $L_1 = 5H$  and  $L_2 = 15H$  are connected in parallel with opposing mutual inductance  $M = 5H$ ?

- b) Derive the expression of the coefficient of coupling for the coupled circuit. 6 Marks L2 CO4 PO2

(OR)

8. a) Define and explain self and mutual inductance. 6 Marks L2 CO4 PO4  
b) Write the comparison between series resonance and parallel resonance. 6 Marks L2 CO4 PO4

### UNIT-V

9. a) Design a constant  $K$ -high pass filter and explain its design procedure in detail. 6 Marks L2 CO4 PO2

- b) Explain the classification of pass band and stop band in detail. 6 Marks L3 CO4 PO3

(OR)

10. a) Derive necessary expressions for  $m$ -derived high pass filter. 6 Marks L3 CO4 PO4  
b) Design a band elimination filter and explain its design procedure in detail. 6 Marks L2 CO4 PO1

