

**SREE VIDYANIKETHAN ENGINEERING COLLEGE**

(An Autonomous Institution, Affiliated to JNTUA, Ananthapuramu)

**I B.Tech I Semester (SVEC-19) Regular Examinations December - 2019****BASIC ELECTRICAL AND ELECTRONICS ENGINEERING****[Electrical and Electronics Engineering, Electronics and Communication Engineering,  
Electronics and Instrumentation Engineering]**

Time: 3 hours

Max. Marks: 60

**Answer One Question from each Unit****All questions carry equal marks****UNIT-I**

- |    |    |  |         |    |     |     |
|----|----|--|---------|----|-----|-----|
| 1. | a) | Classify different types of network elements.              | 6 Marks | L4 | CO1 | PO2 |
|    | b) | Define RMS value and obtain the RMS value for a sine wave. | 6 Marks | L1 | CO1 | PO1 |

**(OR)**

- |    |    |  |         |    |     |     |
|----|----|--|---------|----|-----|-----|
| 2. | a) | State Ohm's law and mention the limitations of it.   | 6 Marks | L1 | CO1 | PO2 |
|    | b) | Define the following:                                | 6 Marks | L1 | CO1 | PO1 |
|    |    | i) Real power ii) Reactive power iii) Apparent power |         |    |     |     |

**UNIT-II**

- |    |    |  |         |    |     |     |
|----|----|--|---------|----|-----|-----|
| 3. | a) | Classify the circuit breakers and write the list of parts of a MCB.  | 6 Marks | L4 | CO2 | PO2 |
|    | b) | Discuss the various causes of low power factor. Explain briefly any one of the method to improve the power factor. | 6 Marks | L3 | CO2 | PO1 |

**(OR)**

- |    |    |  |         |    |     |     |
|----|----|--|---------|----|-----|-----|
| 4. | a) | Draw the layout of typical thermal power plant and explain features. | 6 Marks | L2 | CO2 | PO1 |
|    | b) | Distinguish between Inverter and UPS with neat diagrams.             | 6 Marks | L2 | CO2 | PO2 |

**UNIT-III**

- |    |    |  |         |    |     |     |
|----|----|--|---------|----|-----|-----|
| 5. | a) | Describe slip of induction motor. Why induction motor cannot run at synchronous speed? | 6 Marks | L2 | CO3 | PO1 |
|    | b) | Develop torque-slip characteristics of a 3-phase induction motor and explain.          | 6 Marks | L3 | CO3 | PO3 |

**(OR)**

- |    |    |   |         |    |     |     |
|----|----|---|---------|----|-----|-----|
| 6. | a) | Explain the construction and working principle of a single-phase transformer. | 6 Marks | L2 | CO3 | PO3 |
|    | b) | Categorize single-phase induction motors and list out their applications.     | 6 Marks | L4 | CO3 | PO1 |

**UNIT-IV**

- |    |    |   |         |    |     |     |
|----|----|---|---------|----|-----|-----|
| 7. | a) | Elucidate, how can be a Zener diode used as a voltage regulator.                | 6 Marks | L3 | CO4 | PO2 |
|    | b) | Illustrate the input and output characteristics of BJT in three configurations. | 6 Marks | L3 | CO4 | PO2 |

**(OR)**

- |    |    |  |         |    |     |     |
|----|----|--|---------|----|-----|-----|
| 8. | a) | Explain the operation of a half-wave rectifier with relevant waveforms. What is its output current when <b>rms</b> input voltage is 220V AC and $R_L = 50 \text{ ohm}$ ? | 6 Marks | L3 | CO4 | PO3 |
|    | b) | List the various rectifier circuits for full wave rectification. Describe their advantages and disadvantages.  | 6 Marks | L1 | CO4 | PO1 |

**UNIT-V**

- |    |    |  |         |    |     |     |
|----|----|--|---------|----|-----|-----|
| 9. | a) | Draw the <b>op-amp</b> circuit which acts as differentiator and explain its operation. | 6 Marks | L2 | CO5 | PO1 |
|    | b) | Deduce how an <b>op-amp</b> can be used as an inverting amplifier.                     | 6 Marks | L2 | CO5 | PO1 |

**(OR)**

- |     |    |  |         |    |     |     |
|-----|----|--|---------|----|-----|-----|
| 10. | a) | Compare the ideal and practical characteristics of <b>op-amp</b> . | 6 Marks | L3 | CO5 | PO1 |
|     | b) | Explain how an <b>op-amp</b> can be used as an adder.              | 6 Marks | L2 | CO5 | PO2 |

