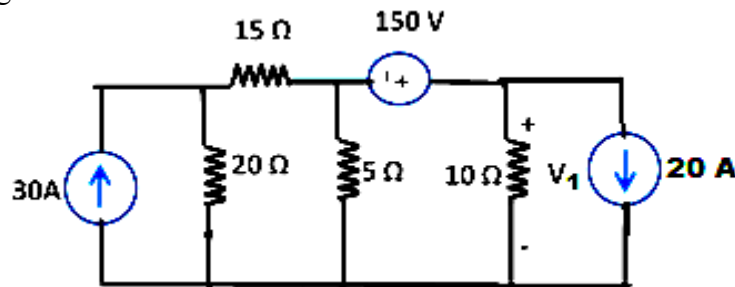


SREE VIDYANIKETHAN ENGINEERING COLLEGE


(An Autonomous Institution, Affiliated to JNTUA, Ananthapuramu)

I B.Tech I Semester (SVEC-16) Regular/Supplementary Examinations December - 2018**ELECTRICAL CIRCUITS****[Electrical and Electronics Engineering]****Time: 3 hours****Max. Marks: 70****Answer One Question from each Unit
All questions carry equal marks****UNIT-I**


- 1 a) Compute the voltage across 10Ω resistor V_1 , using nodal analysis for the circuit shown in figure 7 Marks




- b) Use a series of source transformations to find the voltage V in the circuit shown in figure. 7 Marks

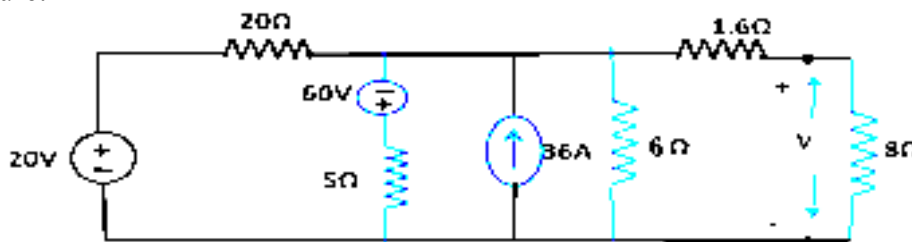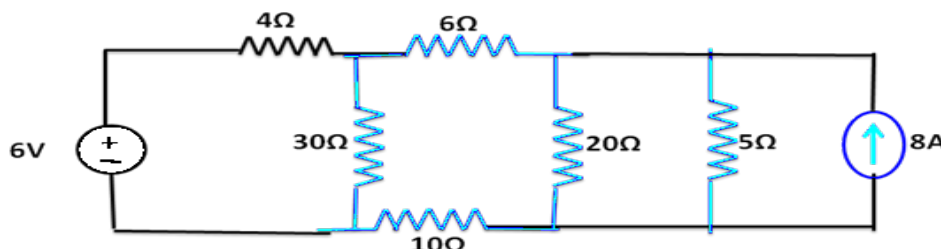**(OR)**


- 2 a) For the circuit shown in figure, use a series of source transformations to find the power associated with 6V source. 7 Marks



- b) Compute the voltage across the 7Ω resistor, using mesh analysis for the circuit shown in figure 7 Marks

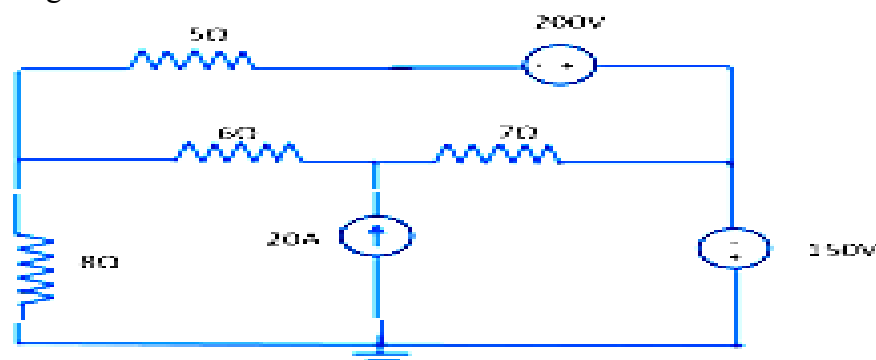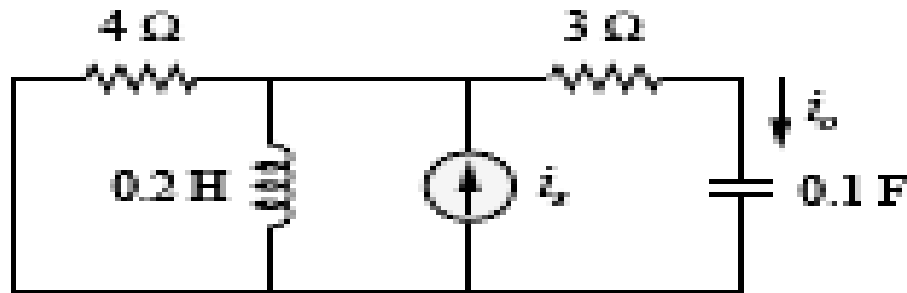
**UNIT-II**

- 3 a) An RLC series circuit has $R = 4\Omega$ and $L = 25\text{mH}$. 7 Marks
 i) Calculate the value of C that will produce a quality factor of 50.
 ii) Find ω_1 and ω_2 .
 iii) Determine the average power dissipated at $\omega = \omega_0, \omega_1, \omega_2$.
 Take $V_m = 100\text{ V}$.
 b) If $i_s = 20 \sin(10t + 15^\circ)\text{ A}$ in the circuit shown in figure, compute the current passing through capacitor i_0 . 7 Marks




(OR)

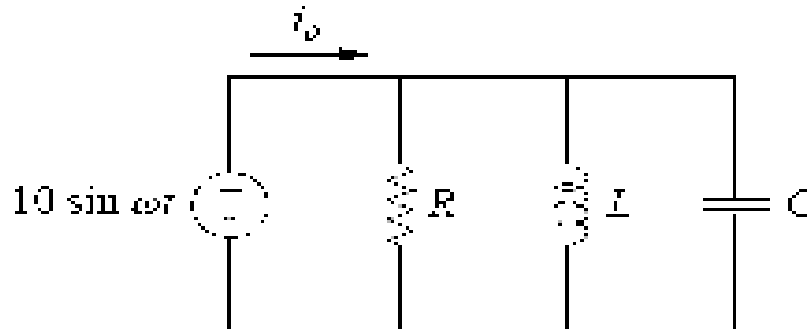- 4 a) In the parallel RLC circuit of figure, let $R = 8\text{k}\Omega$, $L = 0.2\text{mH}$ and $C = 8\mu\text{F}$. 7 Marks
 i) Calculate ω_0 , Q and Band width.
 ii) Find ω_1 and ω_2
 iii) Determine the power dissipated at ω_0, ω_1 and ω_2 .




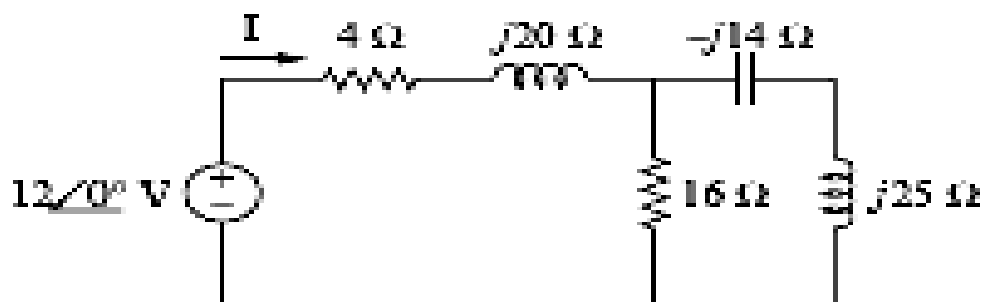- b) Compute the circuit impedance and current in all the elements of circuit shown in figure. 7 Marks



UNIT-III

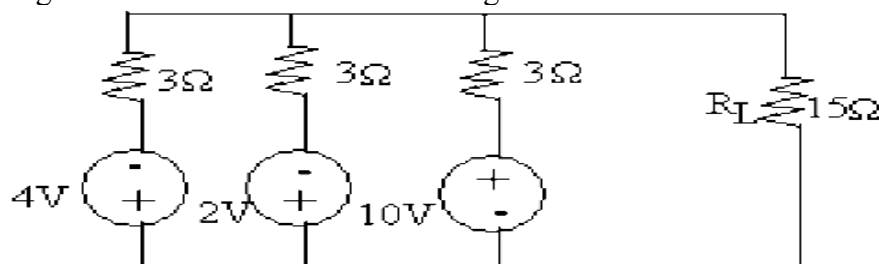- 5 a) State and explain Millman's theorem. 7 Marks
 b) Find the current through load resistance R_L and also find the voltage drop across load using Millman's theorem as shown in figure. 7 Marks




(OR)

- 6 a) State and explain maximum power transfer theorem and derive the necessary 6 Marks

conditions for maximum power transfer for a DC excitations.


- b) Find the current i in the circuit shown in figure using superposition theorem.

8 Marks

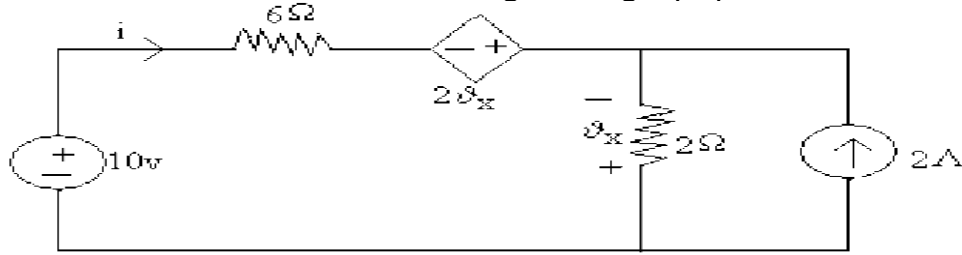


UNIT-IV

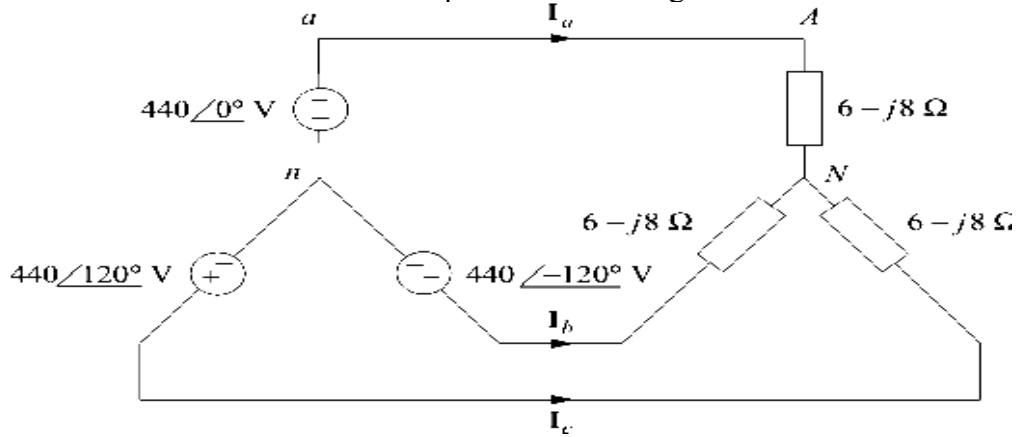- 7 a) Derive the relation between line and phase voltages of wye connected polyphase system. 6 Marks
b) Obtain the line currents in the three-phase circuit of figure. 8 Marks




(OR)

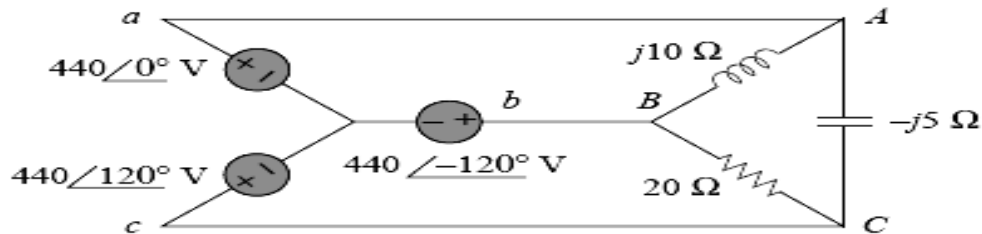- 8 a) Derive the relationship between line and phase quantities (both voltages and currents) in balanced ∇ - ∇ polyphase systems with the phasor diagram. 7 Marks
b) Refer to the unbalanced circuit shown in figure, calculate: (i) the line currents 7 Marks
(ii) the real power, reactive power and apparent power absorbed by the load.




UNIT-V

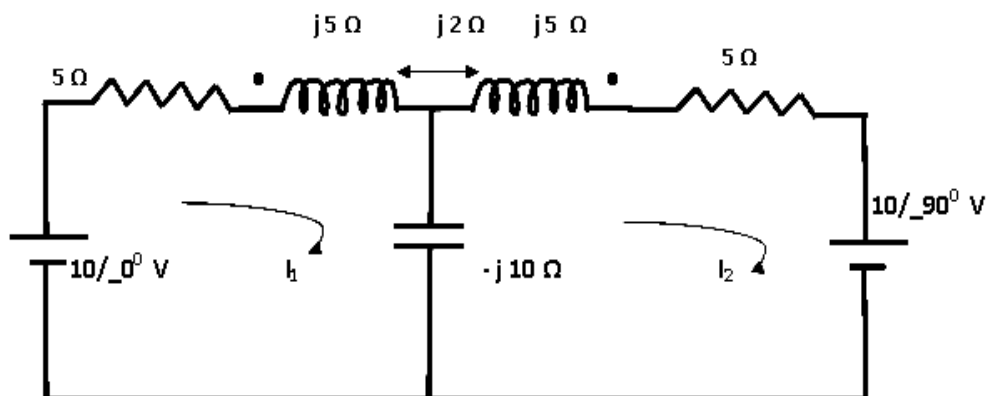- 9 a) For the circuit shown in figure, find the loop currents for the coupled circuits. 7 Marks




- b) Determine the phasor currents I_1 and I_2 in the circuit of the figure .

7 Marks

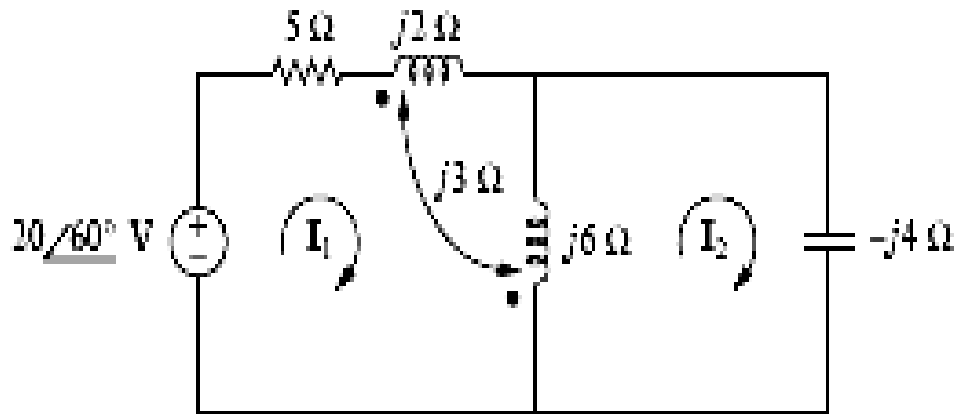

(OR)

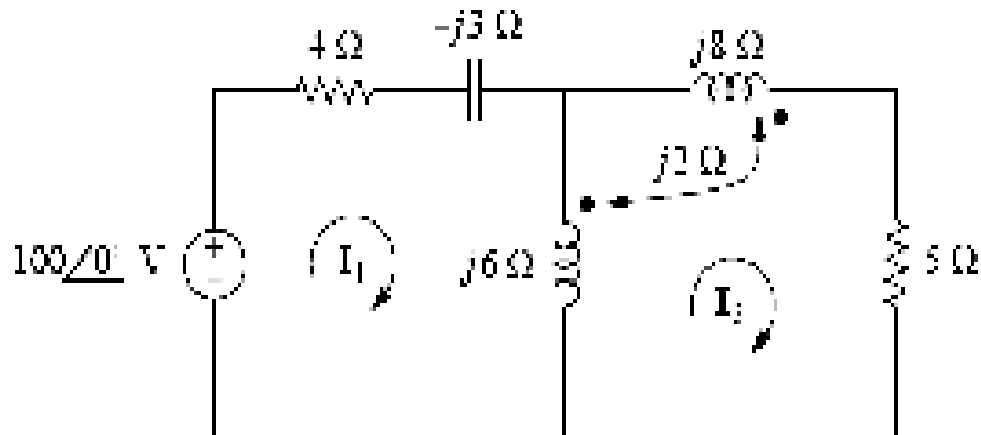- 10 a) Compute the mesh currents shown in figure and also find the voltage across $j8\Omega$ inductor. 7 Marks



- b) Write the mesh equations for the network shown in figure and determine the current through 5Ω resistor. 7 Marks

