

**SREE VIDYANIKETHAN ENGINEERING COLLEGE**

(An Autonomous Institution, Affiliated to JNTUA, Ananthapuramu)

**I B.Tech II Semester (SVEC-16) Regular/Supplementary Examinations June - 2018****ELECTRONIC DEVICES AND CIRCUITS****[Electrical and Electronics Engineering, Electronics and Communication Engineering,  
Electronics and Instrumentation Engineering]**

Time: 3 hours

Max. Marks: 70

**Answer One Question from each Unit.****All questions carry equal marks.****UNIT-I**

- 1 a) Explain the working of bridge rectifier with neat suitable diagram. 7 Marks
- b) Define depletion region at p-n junction. What is the effect of forward and reverse biasing of p-n junction on depletion region? Explain with necessary diagrams. 7 Marks

**(OR)**

- 2 a) Derive the expression for  $I_{dc}$  and  $I_{rms}$  for half-wave rectifier. 8 Marks
- b) A half-wave rectifier circuit supplies 100mA DC to a  $250\Omega$  load. Find the DC output voltage, PIV rating of a diode and the r.m.s. voltage for the transformer supplying the rectifier. 6 Marks

**UNIT-II**

- 3 a) Explain how transistor works as an amplifier. 6 Marks
- b) Explain the output characteristics of a transistor in CB configuration. 8 Marks

**(OR)**

- 4 a) Compare the performance of BJT as an amplifier in CE, CB and CC configurations. 5 Marks
- b) A CE transistor amplifier with voltage divider bias circuit is designed to establish the quiescent point at  $V_{CE} = 12V$ ,  $I_C = 2mA$  and stability factor  $S \leq 5.1$ . If  $V_{CC} = 24V$ ,  $V_{BE} = 0.7V$ ,  $\beta = 50$  and  $R_C = 4.7K\Omega$ , determine the values of resistors  $R_E$ ,  $R_1$  and  $R_2$ . 9 Marks

**UNIT-III**

- 5 a) Explain the concept of Millers theorem and its applications. 8 Marks
- b) Compare enhancement and depletion modes of a MOSFET with the help of its characteristics and construction. 6 Marks

**(OR)**

- 6 Draw the circuit diagram and small signal equivalent of CB amplifier using accurate h-parameter model. Derive expressions for  $A_v$ ,  $A_i$ ,  $R_i$  and  $R_o$ . 14 Marks

**UNIT-IV**

- 7 a) Compare and contrast BJT and FET. 6 Marks
- b) Show that the transconductance  $g_m$  of a JFET is related to the drain current  $I_{DS}$  by 8 Marks

$$g_m = \frac{2}{|V_p|} \sqrt{I_{DS} \cdot I_{DSS}}$$

**(OR)**

- 8 Sketch the basic structure of an n-channel junction field effect transistor and explain its working with the help of drain characteristics. 14 Marks

**UNIT-V**

- 9 What is the photodiode? Explain its principle of operation and applications in detail. 14 Marks

**(OR)**

- 10 Explain the characteristics of UJT. Indicate the negative resistance region. 14 Marks

