

SREE VIDYANIKETHAN ENGINEERING COLLEGE

(An Autonomous Institution, Affiliated to JNTUA, Ananthapuramu)

II B.Tech I Semester (SVEC-19) Regular Examinations February – 2021**ELECTRICAL MACHINES-I**
[Electrical and Electronics Engineering]

Time: 3 hours

Max. Marks: 60

Answer One Question from each Unit
All questions carry equal marks**UNIT-I**

1. a) Explain the constructional features of a DC machine with the help of neat sketch. 6 Marks L1 CO1 PO1
- b) An 8 pole, DC shunt generator with 770 wave connected armature conductors and running at 500 r.p.m supplied a load of 12.5Ω resistance at a terminal voltage of 250V. Armature resistance is 0.24Ω and field resistance is 250Ω . Find armature current and induced EMF. Also find the flux per pole. 6 Marks L3 CO1 PO4

(OR)

2. a) Derive the EMF equation of a DC generator. 6 Marks L2 CO1 PO1
- b) A compound generator delivers a load current of 50A at 500V. The resistances are $R_a=0.05\Omega$, $R_{se}=0.064\Omega$ and $R_{sh}=250\Omega$. The brush contact drop is 1 volt/brush. Find the induced EMF and Armature current when the machine connected as:
i) long shunt. ii) short shunt. 6 Marks L3 CO1 PO2

UNIT-II

3. a) What is armature reaction? Describe the effects of armature reaction on the operation of DC machine and how the armature reaction is minimized. 6 Marks L4 CO1 PO1
- b) A 4 pole lap wound generator having 480 armature conductors. Supplies a current of 150A. If the brushes are given a lead of 10° . Calculate demagnetizing amperes turns/pole and cross magnetising ampere turns/pole. 6 Marks L3 CO1 PO1

(OR)

4. a) What is commutation? Explain the methods of improving commutation. 6 Marks L4 CO1 PO3
- b) What are the conditions for voltage build up of a dc shunt generator? 6 Marks L2 CO2 PO2

UNIT-III

5. a) Explain the Speed-Current, Torque-Current and Speed-Torque characteristics of a DC shunt and series motors. 6 Marks L1 CO3 PO3
- b) A 250V shunt motor has an $R_a=0.2\Omega$ and $R_{sh}=250\Omega$. The motor draws 25A runs at 1000 r.p.m. Calculate the speed when the line current is 50A, if armature reaction weakens the field by 3%. Determine the torque in both cases. 6 Marks L3 CO3 PO2

(OR)

6. a) Derive torque equation of a DC motor from first principles. 6 Marks L1 CO3 PO1
- b) A 4 pole series motor has 944 wave connected armature conductors. At a certain load flux per pole is 34.6mwb and the total mechanical torque developed is 209N-m. Calculate the line current taken by the motor and speed at which it will run with an applied voltage of 500V. Total armature resistance is 3Ω . 6 Marks L3 CO3 PO2

UNIT-IV

7. a) Draw the phasor diagram of loads for single phase transformer. 6 Marks L2 CO4 PO2
b) Derive the EMF equation of a single phase transformer. 6 Marks L1 CO4 PO1

(OR)

8. a) Explain clearly how to perform the OC test on single phase transformer. Write the formulae. 6 Marks L3 CO4 PO4
b) A 15KVA, 2200/220V, 50Hz transformer gave the following results. 6 Marks L3 CO4 PO2

OC test (L.V side): $V = 220V$, $I = 2.742A$, $P = 185W$.

SC test (H.V side): $V = 112V$, $I = 6.3A$, $P = 197W$.

Compute the efficiency at full load 0.8 p.f lead.

UNIT-V

9. a) Give the merits and demerits of star delta connected three phase transformers. Explain the function. 6 Marks L2 CO4 PO1
b) Explain about the Scott connection with neat sketch. 6 Marks L3 CO4 PO2
- (OR)**
10. a) Give the merits and demerits of delta connected three phase transformers. Explain the function. 6 Marks L2 CO4 PO1
b) Illustrate the various types of three phase transformers connections. 6 Marks L1 CO4 PO1

