

SREE VIDYANIKETHAN ENGINEERING COLLEGE

(An Autonomous Institution, Affiliated to JNTUA, Ananthapuramu)

II B.Tech I Semester (SVEC-16) Regular/Supplementary Examinations November - 2018**ELECTRICAL AND ELECTRONICS MEASUREMENTS****[Electronics and Instrumentation Engineering]****Time: 3 hours****Max. Marks: 70****Answer One Question from each Unit****All questions carry equal marks****UNIT-I**

- | | | | | |
|---|----|---|-----|---------|
| 1 | a) | What is the reason behind the oscillations of the pointer in a PMMC when switch is closed and name some mechanism to reduce the oscillations? | CO1 | 7 Marks |
| | b) | Explain about PMMC instrument as an ammeter. How it can be used for AC? Explain in detail. | CO1 | 7 Marks |

(OR)

- | | | | | |
|---|----|---|-----|---------|
| 2 | a) | Discuss in details the types of errors and their causes in Moving Iron Instrument. | CO2 | 7 Marks |
| | b) | Design a multi-range ammeter for the ranges 10mA, 50mA and 75mA using a D'Arsonval movement having an internal coil resistance of 50Ω at a maximum current of 1mA. | CO2 | 7 Marks |

UNIT-II

- | | | | | |
|---|----|---|-----|---------|
| 3 | a) | "Using individual VOLTMETER and AMMETER is not an advisable to measure the power delivered to the load". Justify with mathematical expressions. | CO3 | 7 Marks |
| | b) | Compare the AC potentiometer with the DC potentiometer. | CO4 | 7 Marks |

(OR)

- | | | | | |
|---|--|---|-----|----------|
| 4 | | Using the Phasor diagram of Single Phase Induction type energy meter derive the expression of electrical energy consumed. List out few errors during the process of energy measurement. | CO3 | 14 Marks |
|---|--|---|-----|----------|

UNIT-III

- | | | | | |
|---|----|---|-----|---------|
| 5 | a) | Wheatstone bridges can't be used for low range of resistances. Justify. | CO4 | 7 Marks |
| | b) | Select a suitable bridge to measure low range of resistance, explain its construction and derive the balance condition. | CO5 | 7 Marks |

(OR)

- | | | | | |
|---|----|--|-----|---------|
| 6 | a) | Derive the general equation for balance of an AC bridge and state the two essential conditions to make AC bridge balance. | CO4 | 7 Marks |
| | b) | Discuss the drawbacks of Desauty's bridge and explain how to overcome them with Schering bridge with mathematical support. | CO5 | 7 Marks |

UNIT-IV

- | | | | | |
|---|----|--|-----|---------|
| 7 | a) | Draw the basic block diagram of a digital frequency meter and explain in detail. | CO5 | 7 Marks |
| | b) | Explain the functioning of Stop and Start gate in the time base selector for the measurement of frequency. | CO5 | 7 Marks |

(OR)

- | | | | | |
|---|--|---|-----|----------|
| 8 | | Describe with the help of neat circuit, the application of digital frequency meter for the following measurements
i) Single and Multiple Period measurements.
ii) Time interval measurements. | CO3 | 14 Marks |
|---|--|---|-----|----------|

UNIT-V

- | | | | |
|-------------|---|-----|---------|
| 9 | a) With a neat sketch, explain the LCD technology. | CO1 | 7 Marks |
| | b) Using block diagram, explain the functioning of Digital Storage Oscilloscope. | CO2 | 7 Marks |
| (OR) | | | |
| 10 | a) Write short note on:
i) Magnetic tape recorders. ii) CD/DVD recorders. | CO6 | 7 Marks |
| | b) Elaborate why the study of spectrum analysis so important in analyzing signals. | CO6 | 7 Marks |

